

DIGITAL LOGIC CIRCUITS

Logic Gates

Boolean Algebra

Map Specification

Combinational Circuits


Flip-Flops

Sequential Circuits

Memory Components

Integrated Circuits

BASIC LOGIC BLOCK - GATE -

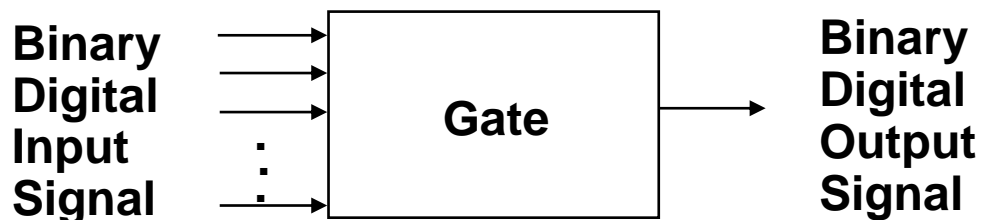

Types of Basic Logic Blocks

- **Combinational Logic Block**

Logic Blocks whose output logic value depends only on the input logic values









- **Sequential Logic Block**

Logic Blocks whose output logic value depends on the input values and the state (stored information) of the blocks

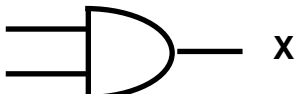Functions of Gates can be described by

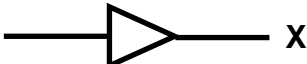- Truth Table
- Boolean Function
- Karnaugh Map

COMBINATIONAL GATES

Name	Symbol	Function	Truth Table															
AND		$X = A \cdot B$ or $X = AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$X = A + B$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
I		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NAND		$X = (AB)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$X = (A + B)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR Exclusive OR		$X = A \oplus B$ or $X = A'B + AB'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR Exclusive NOR or Equivalence		$X = (A \oplus B)'$ or $X = A'B' + AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

LOGIC CIRCUIT DESIGN


Truth Table

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Boolean Function

$F = x + y'z$

Logic Diagram

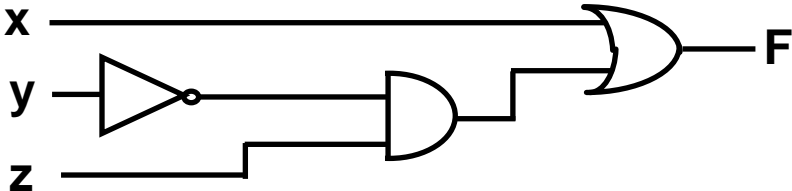

BASIC IDENTITIES OF BOOLEAN ALGEBRA

$$[1] \quad x + 0 = x$$

$$[3] \quad x + 1 = 1$$

$$[5] \quad x + x = x$$

$$[7] \quad x + x' = 1$$

$$[9] \quad x + y = y + x$$

$$[11] \quad x + (y + z) = (x + y) + z$$

$$[13] \quad x(y + z) = xy + xz$$

$$[15] \quad (x + y)' = x'y'$$

$$[17] \quad (x')' = x$$

$$[2] \quad x \cdot 0 = 0$$

$$[4] \quad x \cdot 1 = x$$

$$[6] \quad x \cdot x = x$$

$$[8] \quad x \cdot x' = 0$$

$$[10] \quad xy = yx$$

$$[12] \quad x(yz) = (xy)z$$

$$[14] \quad x + yz = (x + y)(x + z)$$

$$[16] \quad (xy)' = x' + y'$$

[15] and [16] : De Morgan's Theorem

Usefulness of this Table



- Simplification of the Boolean function
 - Derivation of equivalent Boolean functions to obtain logic diagrams utilizing different logic gates
 - Ordinarily ANDs, ORs, and Inverters
 - But a certain different form of Boolean function may be convenient to obtain circuits with NANDs or NORs
- Applications of De Morgans Theorem

$$x'y' = (x + y)'$$

I, AND → NOR

$$x' + y' = (xy)'$$

I, OR → NAND

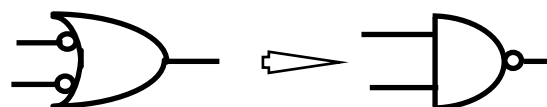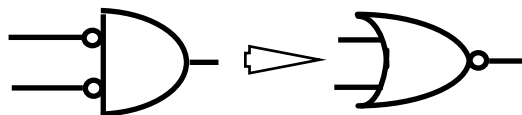

EQUIVALENT CIRCUITS

Many different logic diagrams are possible for a given Function


$$\begin{aligned} F &= ABC + ABC' + A'C \\ &= AB(C + C') + A'C \\ &= AB \cdot 1 + A'C \\ &= AB + A'C \end{aligned}$$

..... (1)

[13] (2)

[7]

[4] (3)

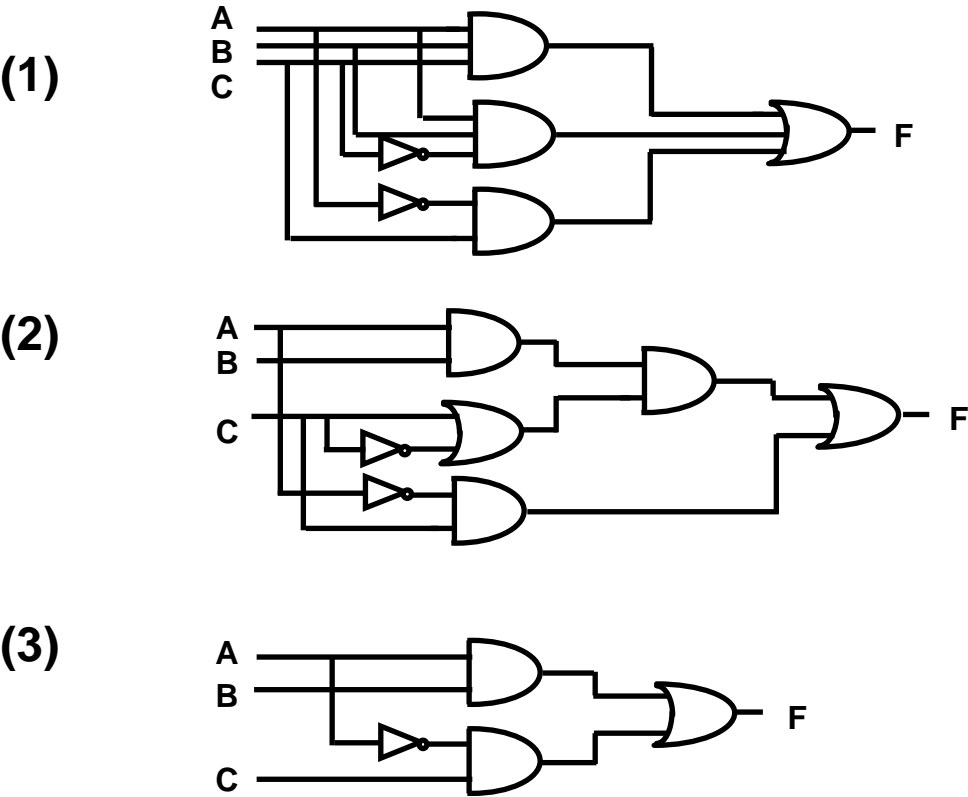

COMPLEMENT OF FUNCTIONS

A Boolean function of a digital logic circuit is represented by only using logical variables and AND, OR, and Invert operators.

→ Complement of a Boolean function

- Replace all the variables and subexpressions in the parentheses appearing in the function expression with their respective complements

$$A, B, \dots, Z, a, b, \dots, z \Rightarrow A', B', \dots, Z', a', b', \dots, z'$$
$$(p + q) \Rightarrow (p + q)'$$

- Replace all the operators with their respective complementary operators


$$\text{AND} \Rightarrow \text{OR}$$
$$\text{OR} \Rightarrow \text{AND}$$

- Basically, extensive applications of the De Morgan's theorem

$$(x_1 + x_2 + \dots + x_n)' \Rightarrow x_1' x_2' \dots x_n'$$

$$(x_1 x_2 \dots x_n)' \Rightarrow x_1' + x_2' + \dots + x_n'$$

SIMPLIFICATION

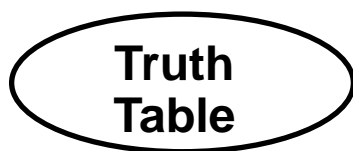

Unique




Many different expressions exist

Simplification from Boolean function

- Finding an equivalent expression that is least expensive to implement
- For a simple function, it is possible to obtain a simple expression for low cost implementation
- But, with complex functions, it is a very difficult task

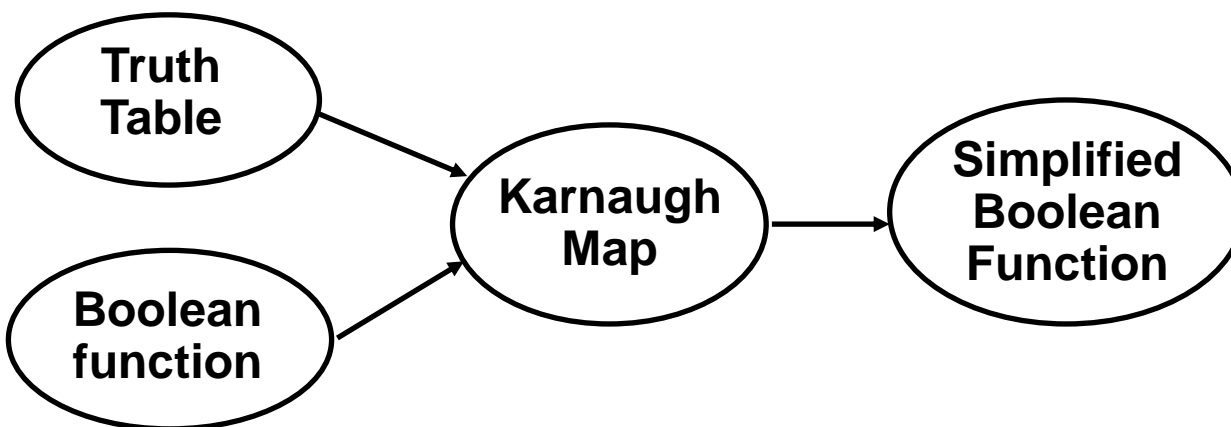Karnaugh Map (K-map) is a simple procedure for simplifying Boolean expressions.




KARNAUGH MAP

Karnaugh Map for an n-input digital logic circuit (n-variable sum-of-products form of Boolean Function, or Truth Table) is

- Rectangle divided into 2^n cells
- Each cell is associated with a *Minterm*
- An output(function) value for each input value associated with a minterm is written in the cell representing the minterm
→ 1-cell, 0-cell



Each Minterm is identified by a decimal number whose binary representation is identical to the binary interpretation of the input values of the minterm.

Karnaugh Map

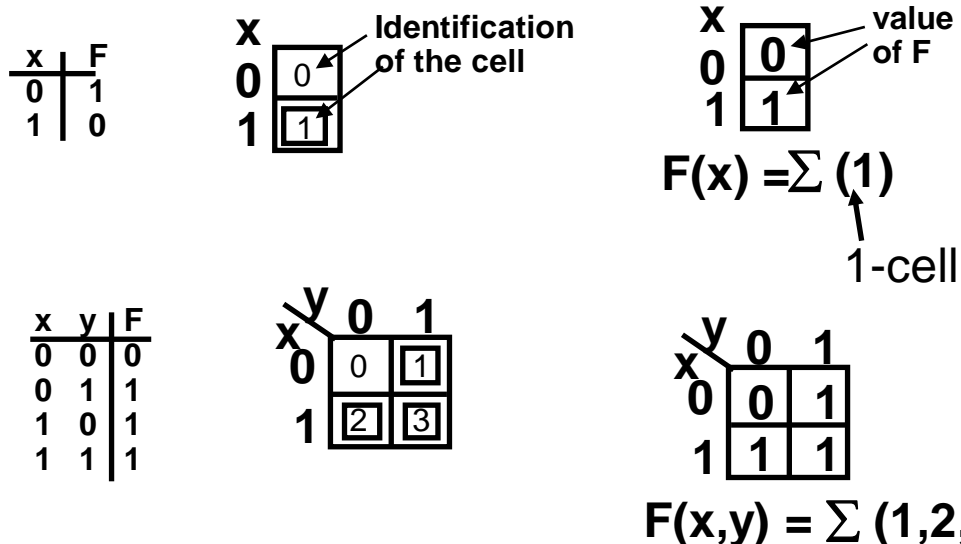



KARNAUGH MAP

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

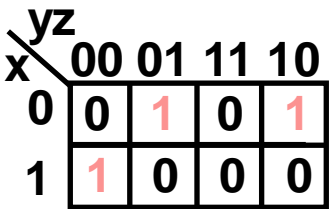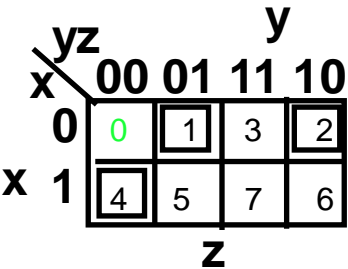

$F(x,y,z) = \sum (1,2,4)$

u	v	w	x	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

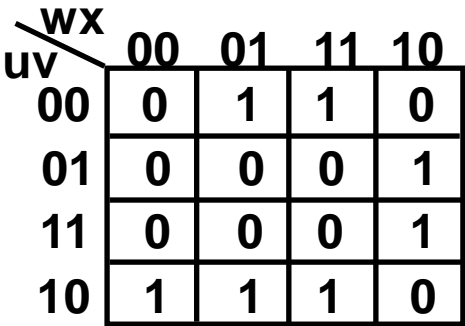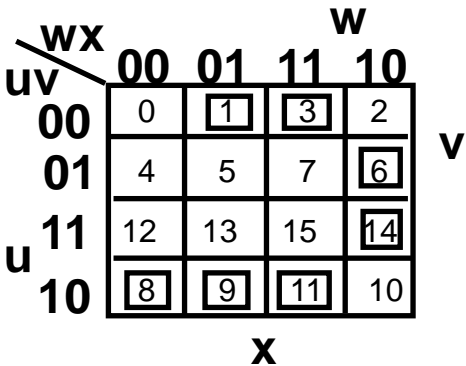

$F(u,v,w,x) = \sum (1,3,6,8,9,11,14)$

MAP SIMPLIFICATION - 2 ADJACENT CELLS -

Rule: $xy' + xy = x(y + y') = x$

Adjacent cells

- binary identifications are different in one bit
 → minterms associated with the adjacent cells have one variable complemented each other

Cells (1,0) and (1,1) are adjacent

Minterms for (1,0) and (1,1) are

$$x \cdot y' \rightarrow x=1, y=0$$

$$x \cdot y \rightarrow x=1, y=1$$

$F = xy' + xy$ can be reduced to $F = x$
 From the map

		y		0	1
		x		0	1
0				0	0
1				1	1

2 adjacent cells xy' and xy
 → merge them to a larger cell x


$$\begin{aligned}
 F(x,y) &= \sum (2,3) \\
 &= xy' + xy \\
 &= x
 \end{aligned}$$

IMPLEMENTATION OF K-MAPS - Product-of-Sums Form -

Logic function represented by a Karnaugh map can be implemented in the form of I-OR-AND


If we implement a Karnaugh map using 0-cells, the complement of F , i.e., F' , can be obtained. Thus, by complementing F' using DeMorgan's theorem F can be obtained

$$F(x,y,z) = (0,2,6)$$

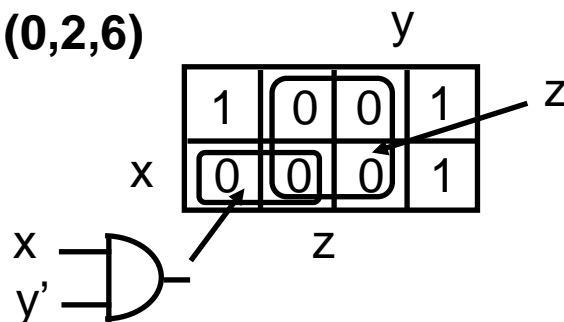

$$F' = xy' + z$$

$$F = (xy')z' = (x' + y)z'$$

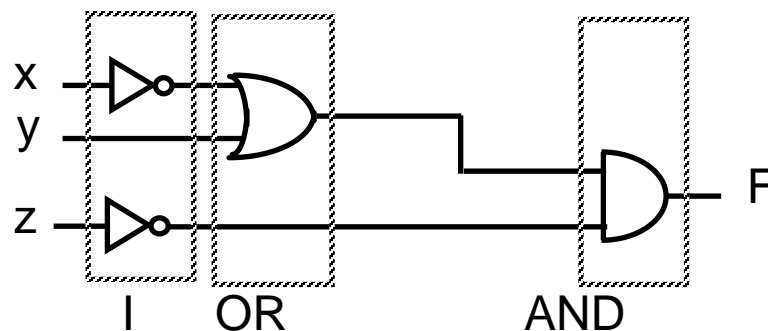



IMPLEMENTATION OF K-MAPS - Don't-Care Conditions -

In some logic circuits, the output responses for some input conditions are don't care whether they are 1 or 0.

In K-maps, don't-care conditions are represented by d's in the corresponding cells.

Don't-care conditions are useful in minimizing the logic functions using K-map.

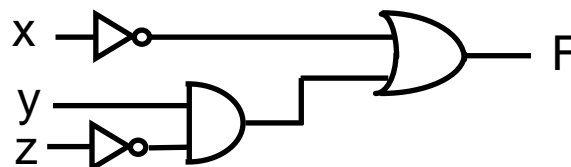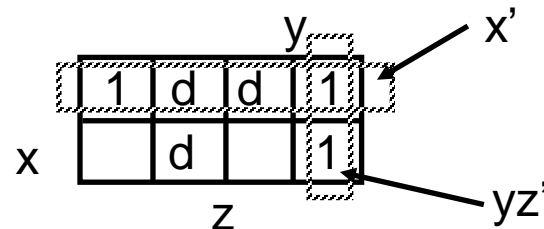- Can be considered either 1 or 0
- Thus increases the chances of merging cells into the larger cells
--> Reduce the number of variables in the product terms



COMBINATIONAL LOGIC CIRCUITS

Half Adder


x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

	y
x	0
	1

$c = xy$

	y
x	0
	1

$s = xy' + x'y$
 $= x \oplus y$

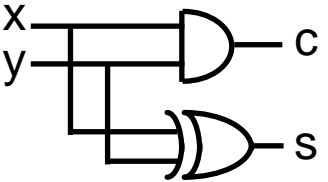

Full Adder

x	y	c_{n-1}	c_n	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

	y
x	0
	0
	1
	0

c_n

	y
x	0
	1
	0
	1


s

$$c_n = xy + xc_{n-1} + yc_{n-1}$$

$$= xy + (x \oplus y)c_{n-1}$$

$$s = x'y'c_{n-1} + x'yc'_{n-1} + xy'c'_{n-1} + xyc_{n-1}$$
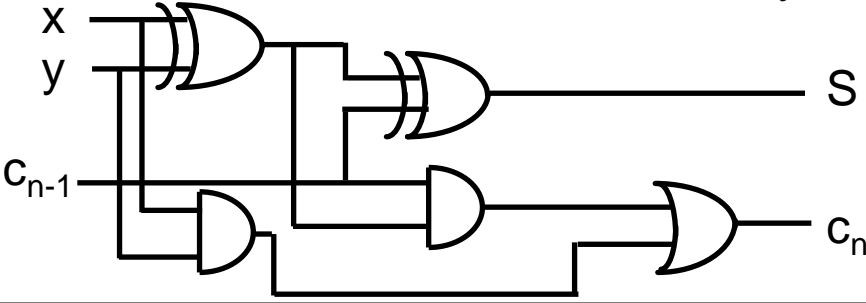
$$= x \oplus y \oplus c_{n-1} = (x \oplus y) \oplus c_{n-1}$$



COMBINATIONAL LOGIC CIRCUITS

Other Combinational Circuits

Multiplexer

Encoder

Decoder

Parity Checker

Parity Generator

etc


Multiplexer

- Definition
- Logic Diagram
- Application


MULTIPLEXER

4-to-1 Multiplexer

Select		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

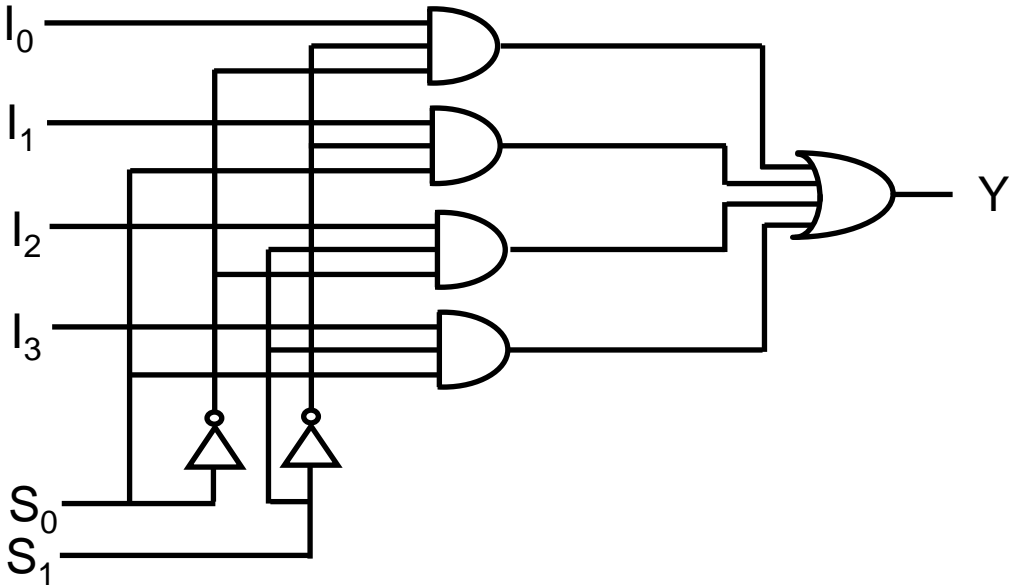


4. Demultiplexers

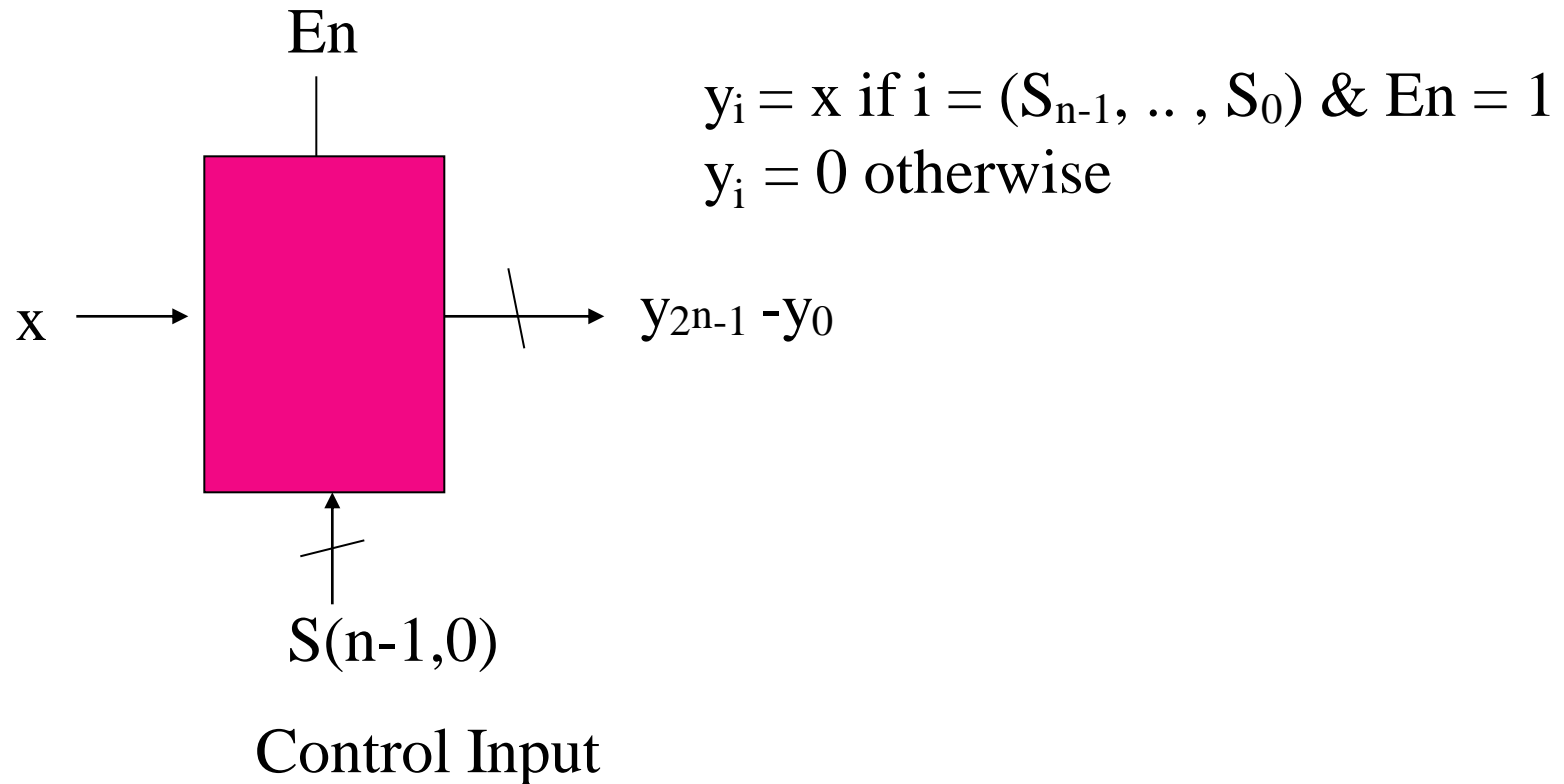

1. Decoder

- Definition
- Logic Diagram
- Application (Universal Set)
- Tree of Decoders

1. Decoder: Definition

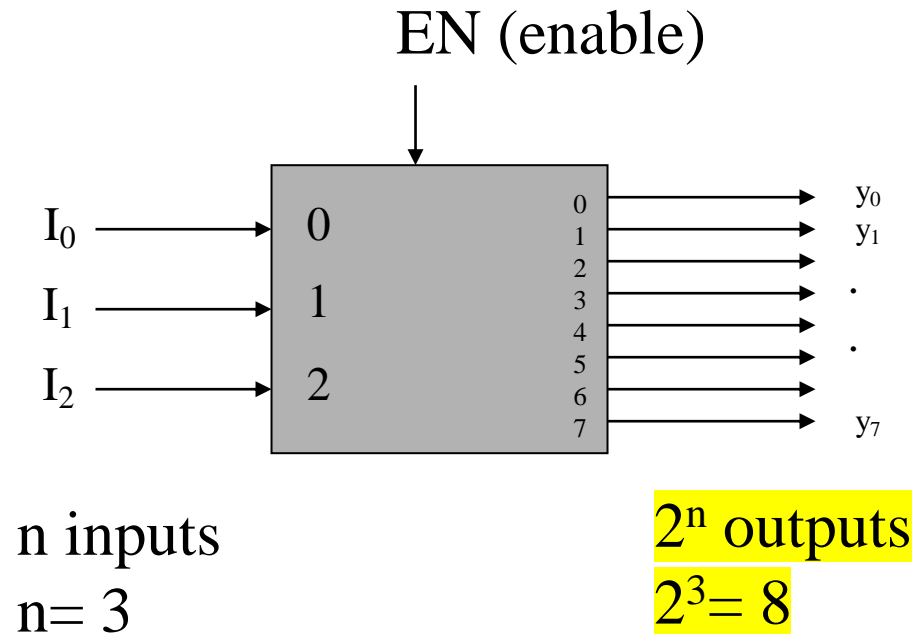


n to 2^n decoder
function:

$$y_i = 1 \text{ if } En = 1 \text{ \& } (I_2, I_1, I_0) = i$$
$$y_i = 0 \text{ otherwise}$$

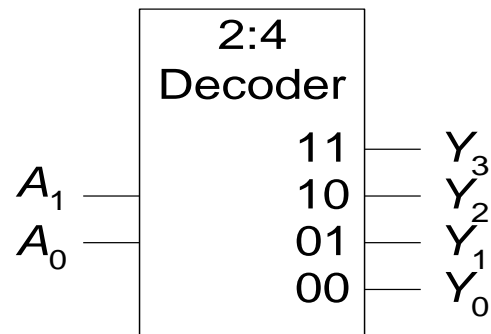
1. Decoder: Definition

- N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder: Logic Diagram

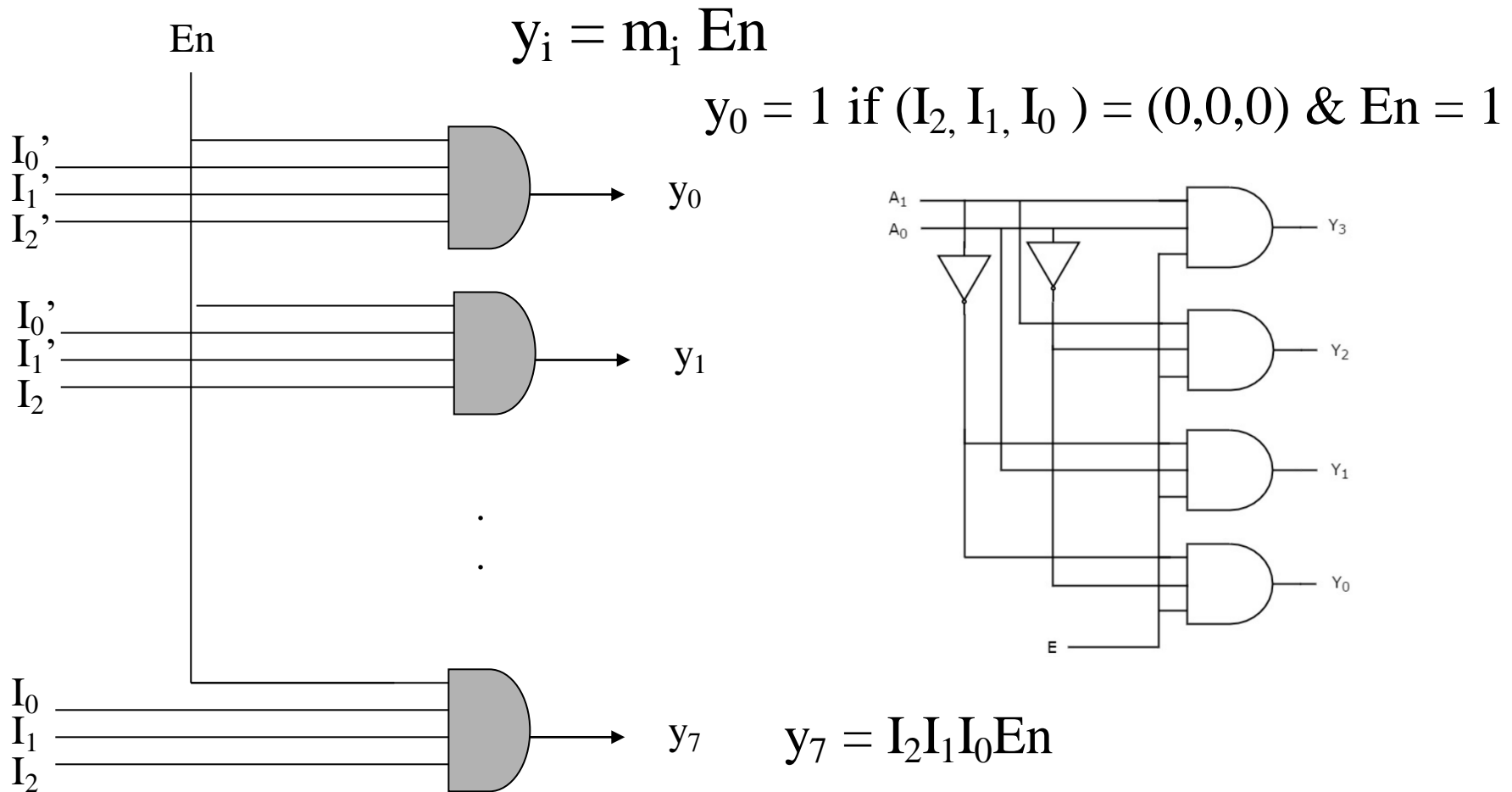


Tree of Decoders

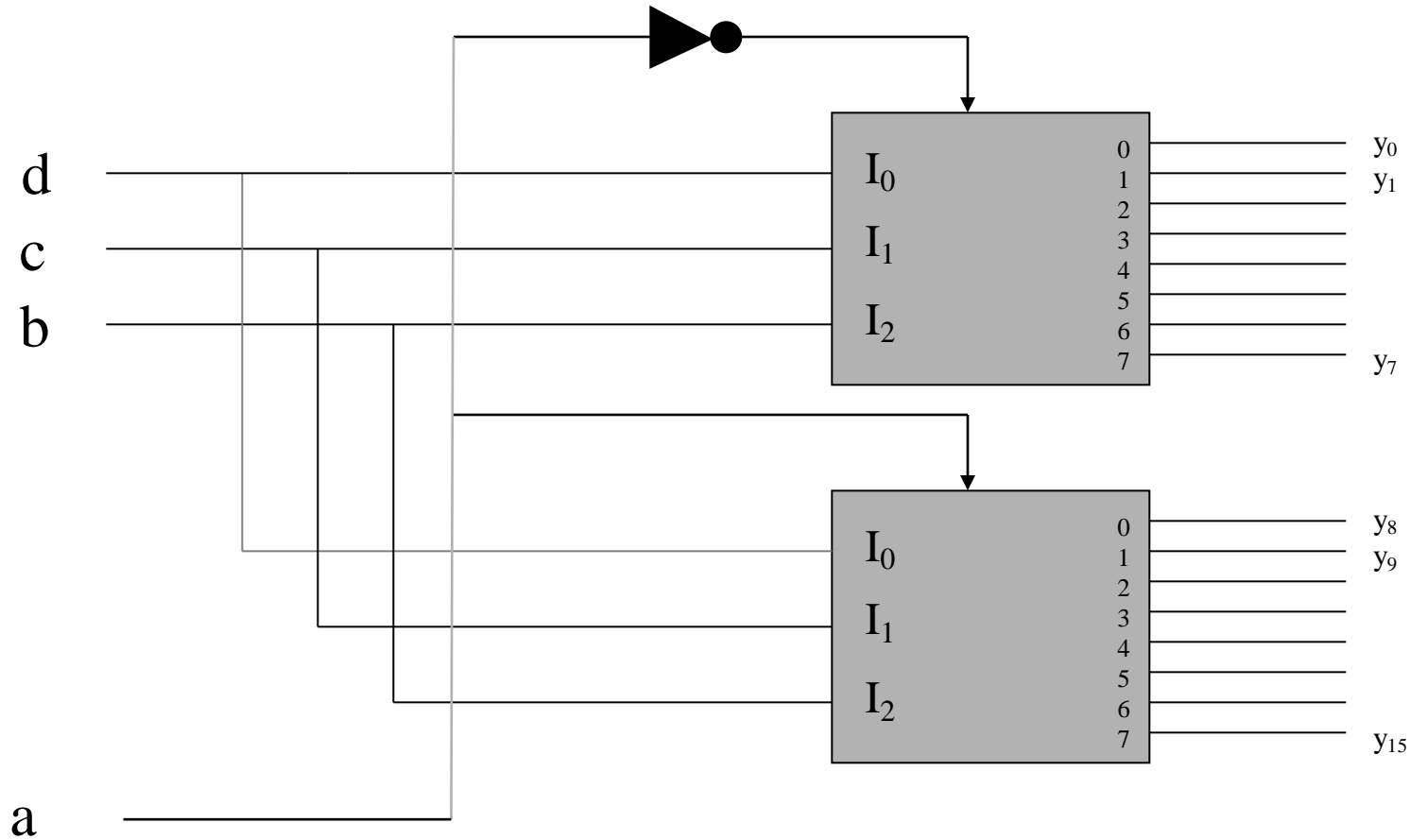Implement a 4- 2^4 decoder with 3- 2^3 decoders.



Tree of Decoders

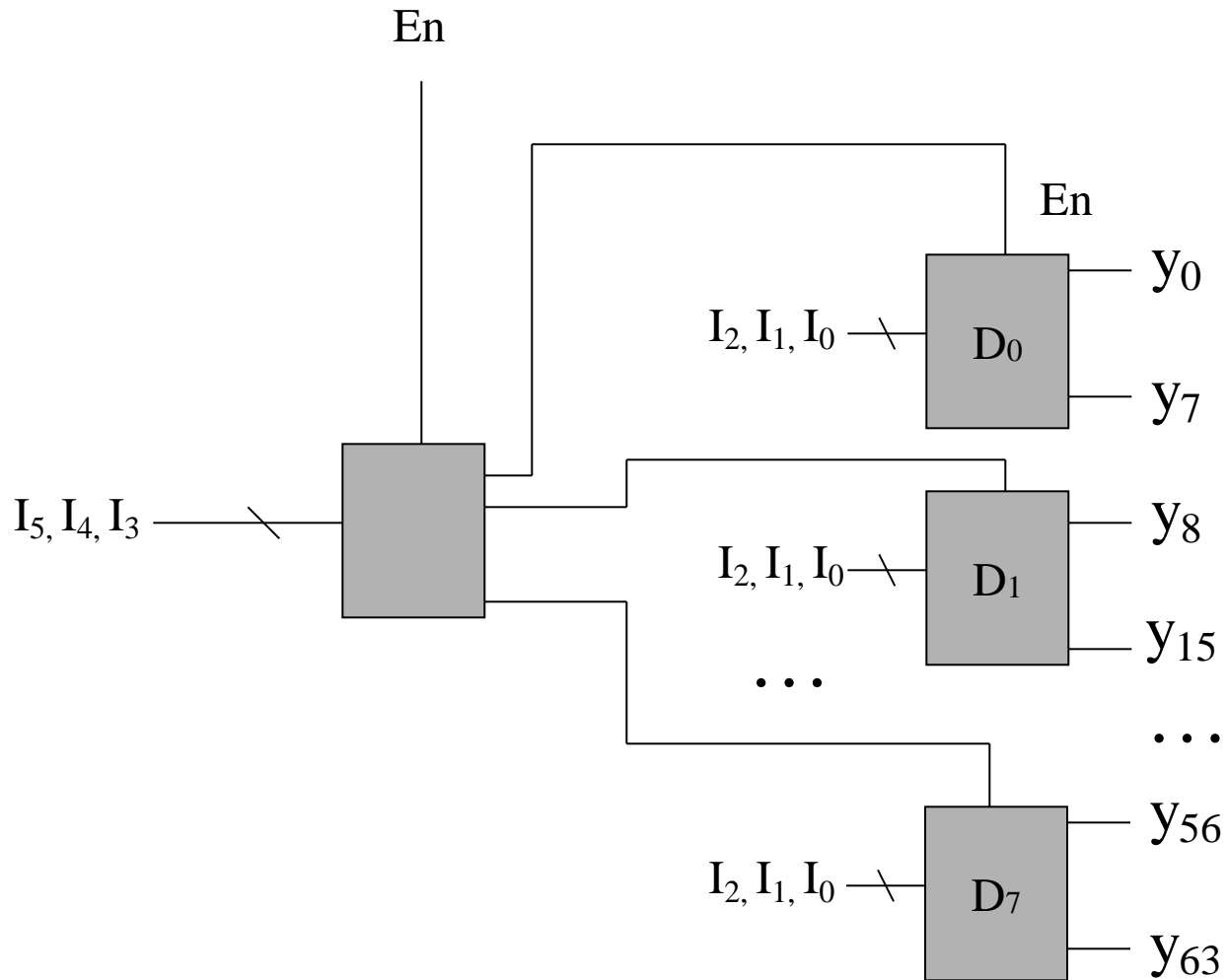Implement a $6\text{-}2^6$ decoder with $3\text{-}2^3$ decoders.



Tree of Decoders


$$\text{Required number of lower order decoders} = \frac{m_2}{m_1}$$

Where,

m_1 is the number of outputs of lower order decoder.

m_2 is the number of outputs of higher order decoder.

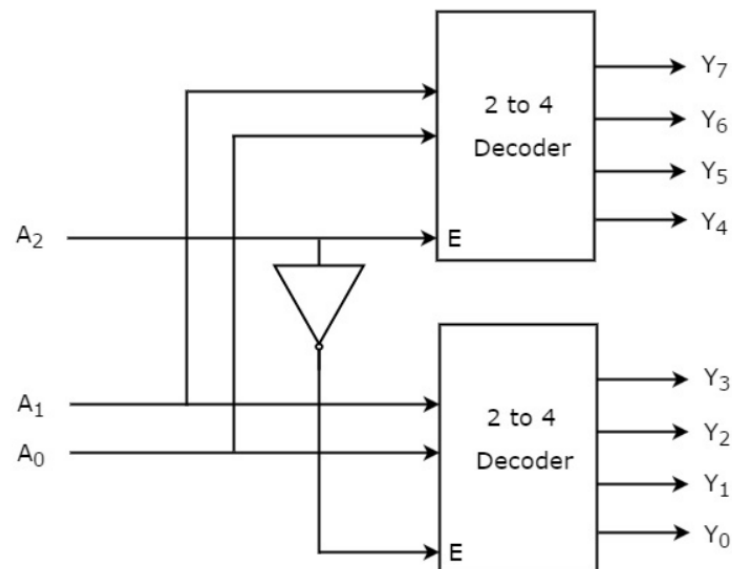
Here, $m_1 = 4$ and $m_2 = 8$. Substitute, these two values in the above formula.




2. Encoder

- Definition
- Logic Diagram
- Priority Encoder

2. Encoder: Definition

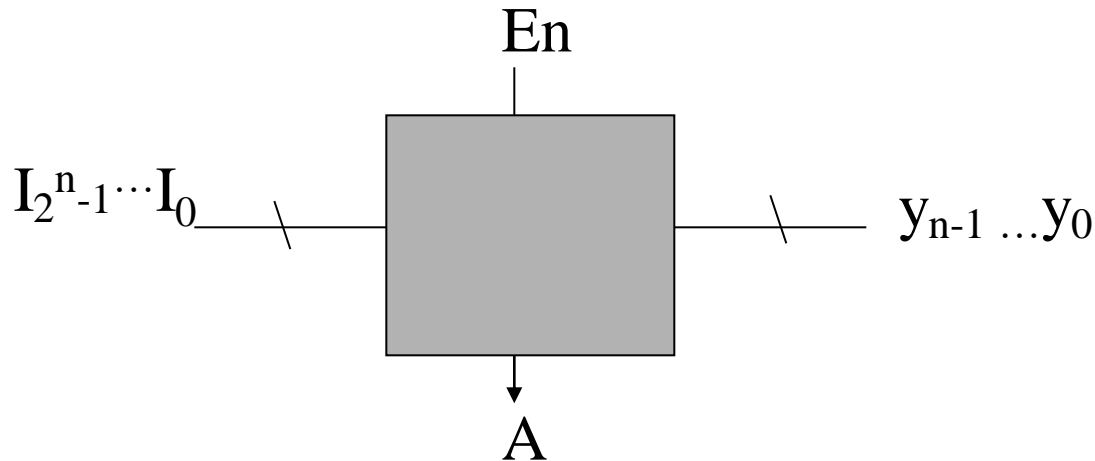

Encoder Description:

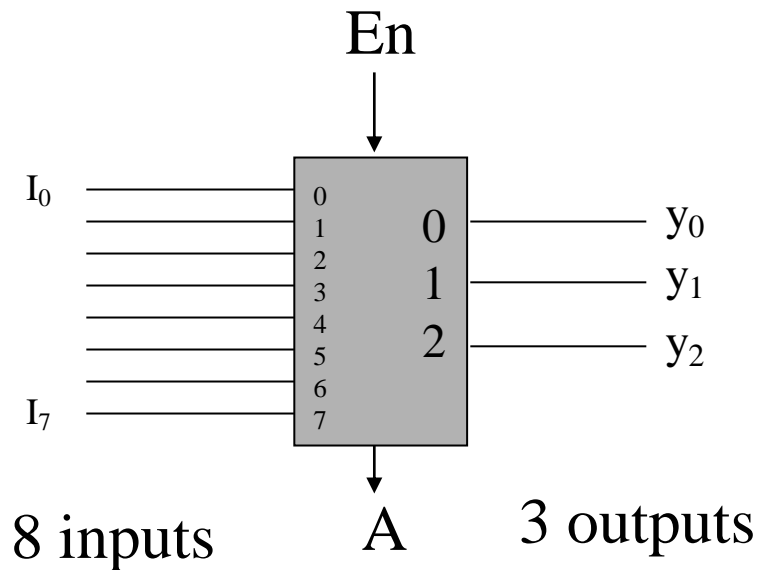

At most one $I_i = 1$.





$(y_{n-1}, \dots, y_0) = i$ if $I_i = 1$ & $En = 1$

$(y_{n-1}, \dots, y_0) = 0$ otherwise.


$A = 1$ if $En = 1$ and one i s.t. $I_i = 1$

$A = 0$ otherwise.

Encoder: Logic Diagram

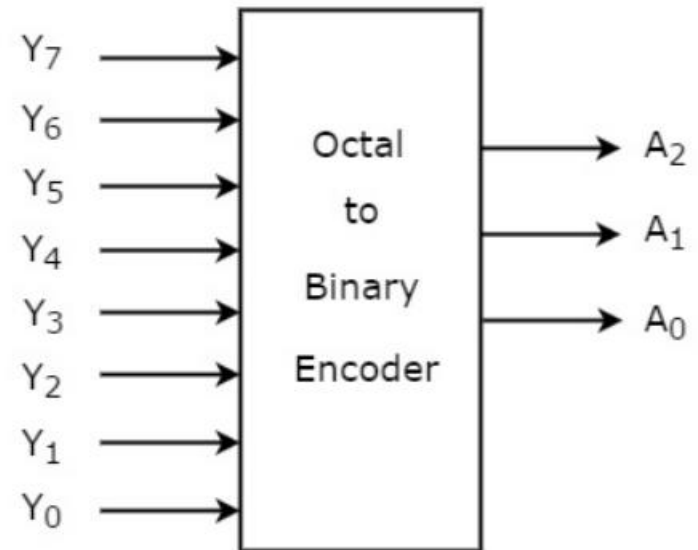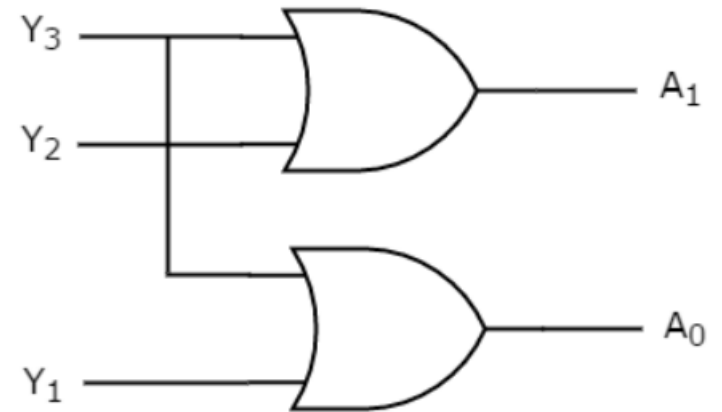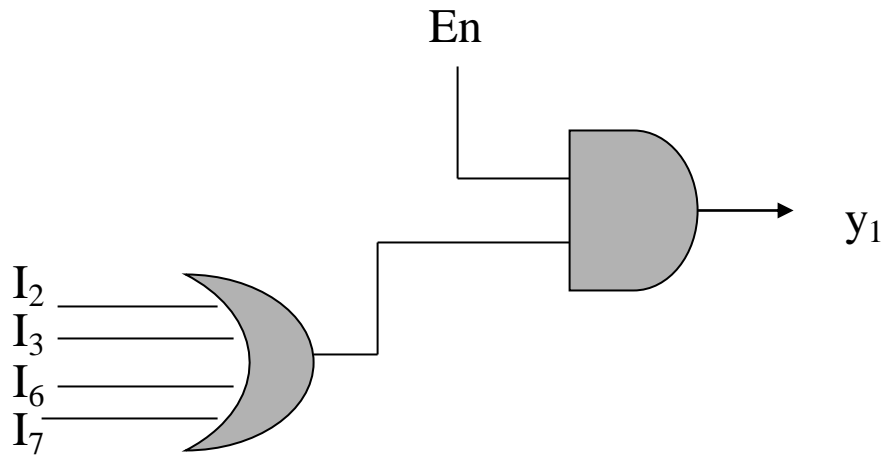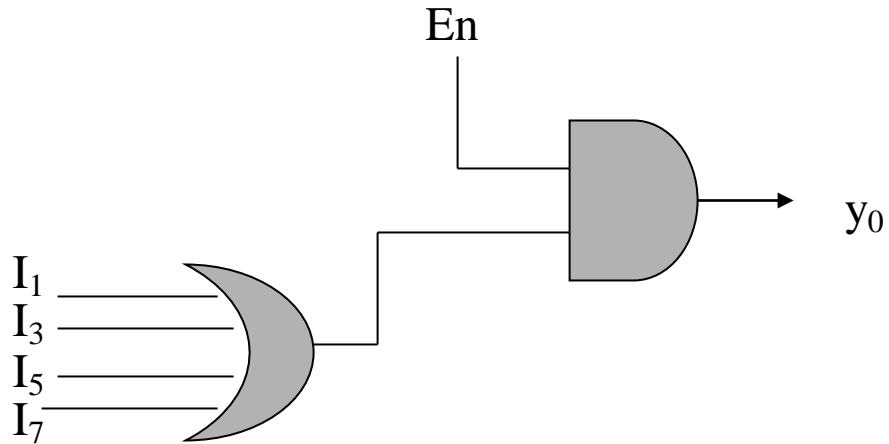


Encoder: Logic Diagram

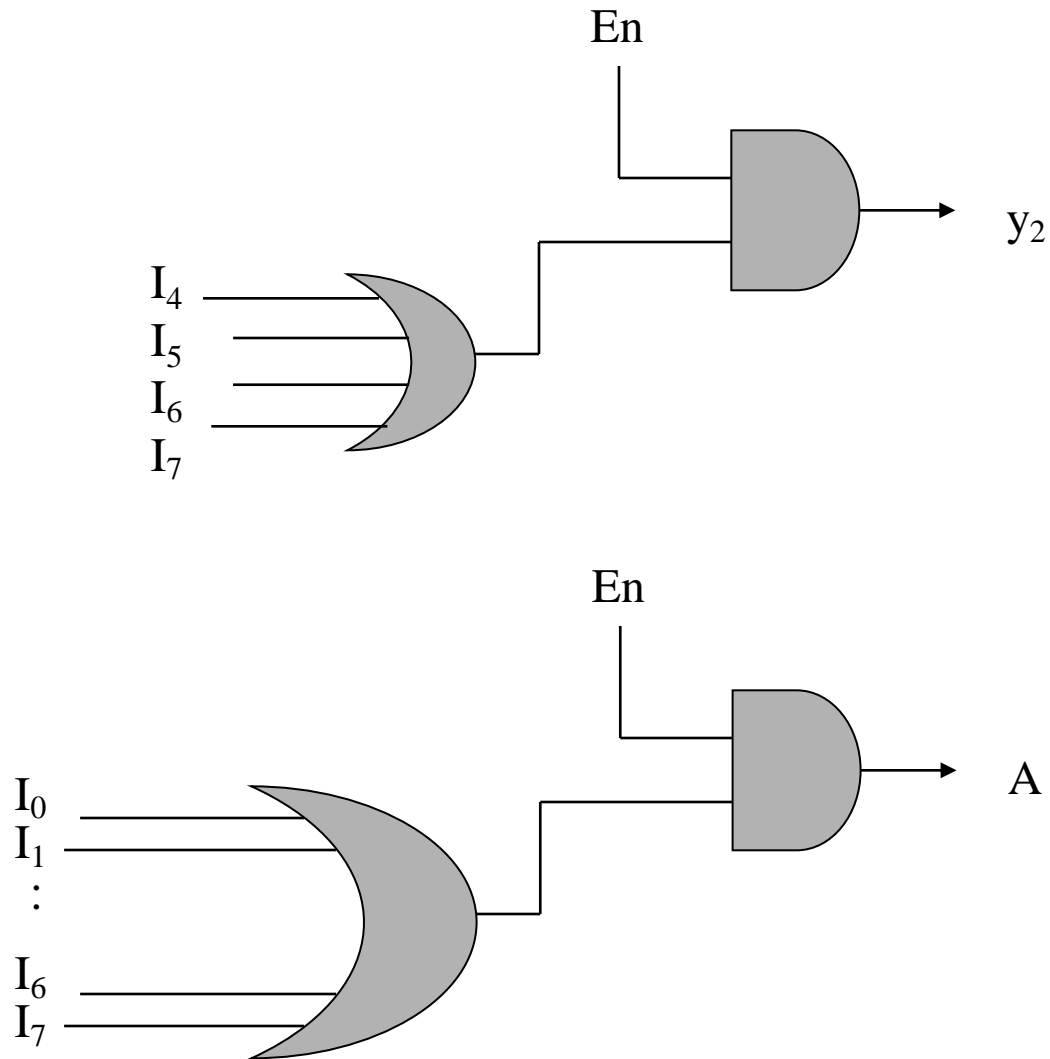


ENCODER/DECODER

Octal-to-Binary Encoder

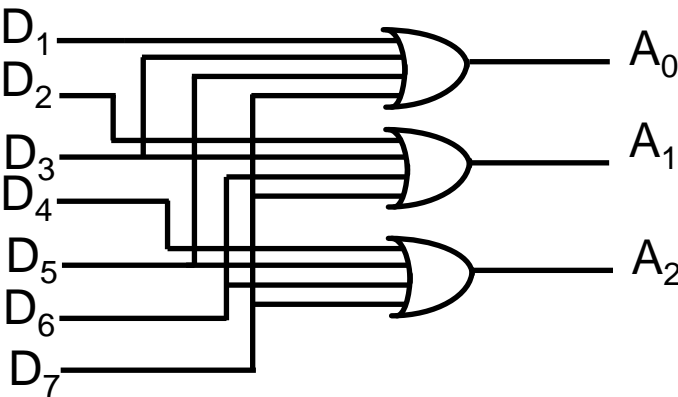


2-to-4 Decoder

E	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	d	d	1	1	1	1

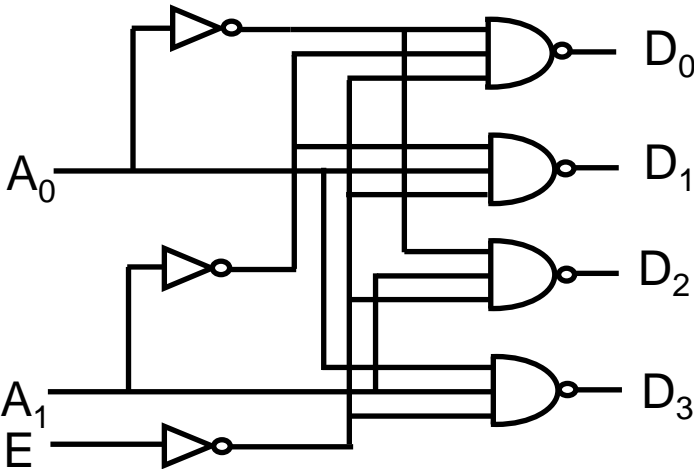

Memory Elements

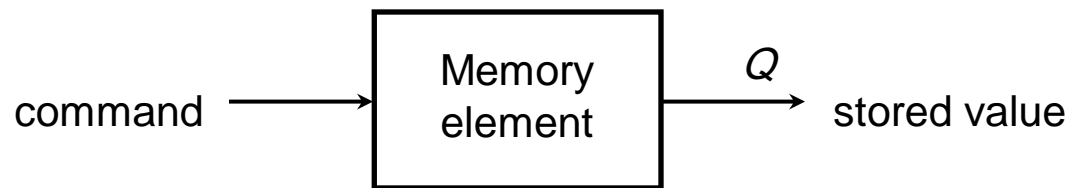- **Memory element**: a device which can remember value indefinitely, or change value on command from its inputs.




- **Characteristic table**:

Command (at time t)	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1


$Q(t)$: current state

$Q(t+1)$ or Q^+ : next state

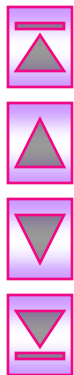


Memory Elements

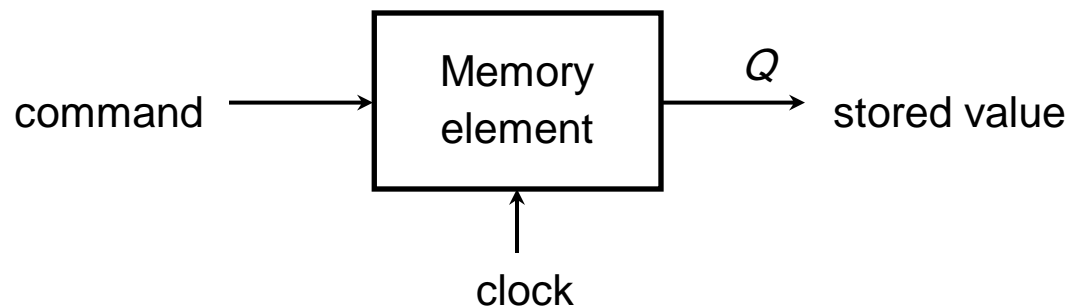- Memory element with clock. Flip-flops are memory elements that change state on clock signals.




- Clock is usually a square wave.

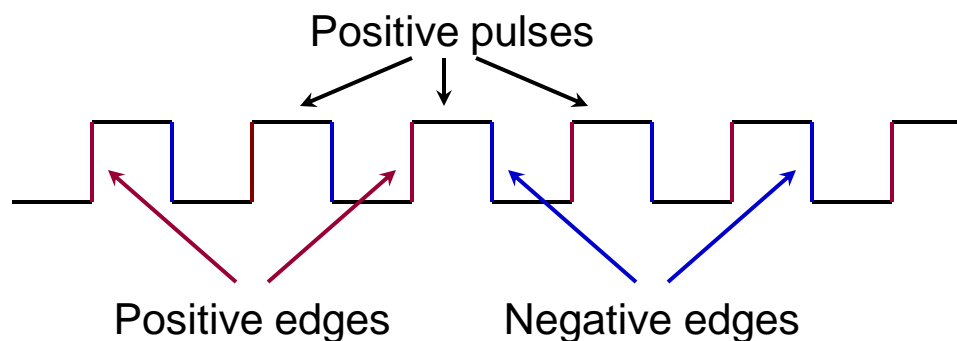

Memory Elements

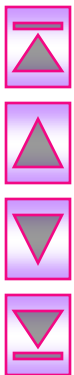- Two types of triggering/activation:
 - ❖ pulse-triggered
 - ❖ edge-triggered
- Pulse-triggered
 - ❖ latches
 - ❖ ON = 1, OFF = 0
- Edge-triggered
 - ❖ flip-flops
 - ❖ positive edge-triggered (ON = from 0 to 1; OFF = other time)
 - ❖ negative edge-triggered (ON = from 1 to 0; OFF = other time)



S-R Latch



- *Complementary* outputs: Q and Q' .
- When Q is HIGH, the latch is in *SET* state.
- When Q is LOW, the latch is in *RESET* state.
- For *active-HIGH input S-R latch* (also known as NOR gate latch),
 - $R=HIGH$ (and $S=LOW$) \Rightarrow RESET state
 - $S=HIGH$ (and $R=LOW$) \Rightarrow SET state
 - both inputs LOW \Rightarrow no change
 - both inputs HIGH \Rightarrow Q and Q' both LOW (invalid)!



S-R Latch



- Characteristics table for active-high input S-R latch:

S	R	Q	Q'	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

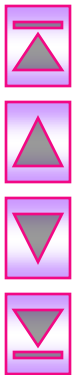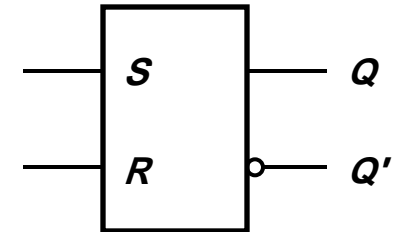




S-R Latch

Active-HIGH input S-R latch

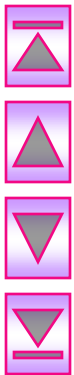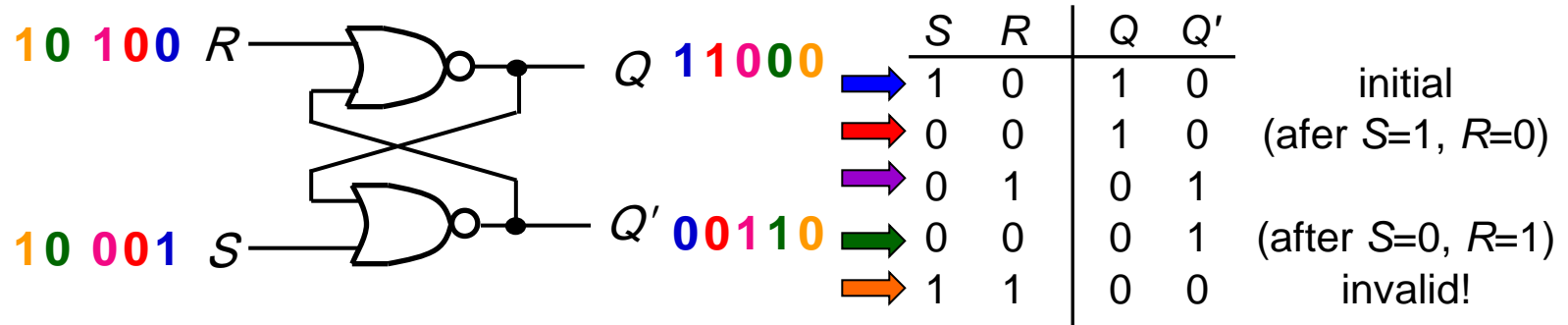

Gated D Latch

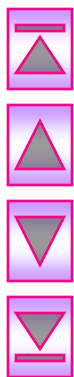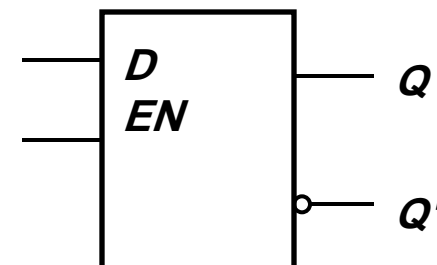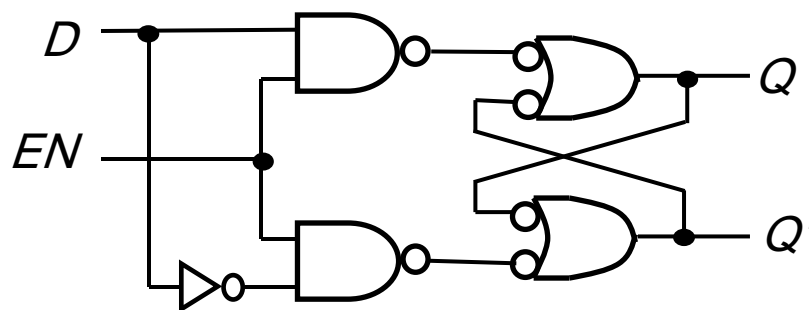- Make R input equal to S' → *gated D latch*.
- D latch eliminates the undesirable condition of invalid state in the S – R latch.




Gated D Latch

- When EN is HIGH,
 - ❖ $D=HIGH \rightarrow$ latch is SET
 - ❖ $D=LOW \rightarrow$ latch is RESET
- Hence when EN is HIGH, Q 'follows' the D (data) input.
- Characteristic table:

EN	D	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change

When $EN=1$, $Q(t+1) = D$

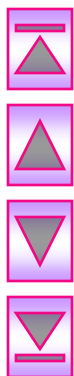

Latch Circuits: Not Suitable


- Latch circuits are not suitable in synchronous logic circuits.
- When the enable signal is active, the excitation inputs are gated directly to the output Q. Thus, any change in the excitation input immediately causes a change in the latch output.
- The problem is solved by using a special timing control signal called a *clock* to restrict the times at which the states of the memory elements may change.



- This leads us to the edge-triggered memory elements called *flip-flops*.


Edge-Triggered Flip-flops

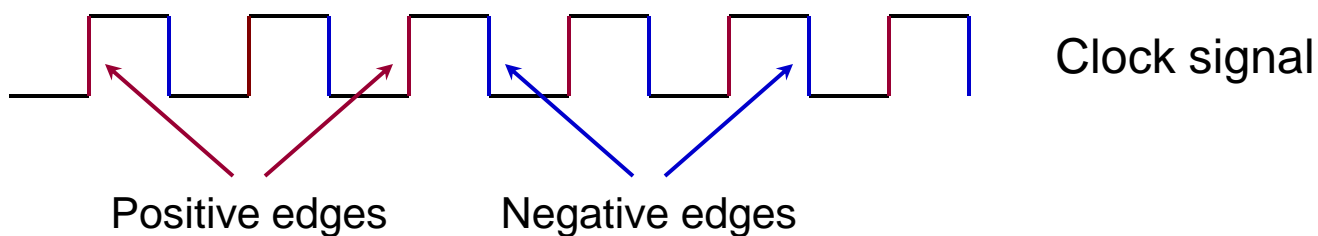- *Flip-flops*: synchronous bistable devices
- Output changes state at a specified point on a triggering input called the *clock*.
- Change state either at the *positive edge* (rising edge) or at the *negative edge* (*falling edge*) of the clock signal.




Edge-Triggered Flip-flops

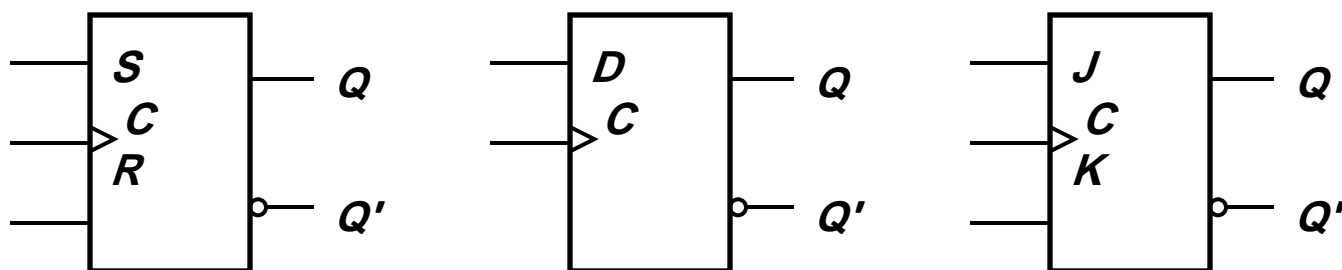- S-R, D and J-K edge-triggered flip-flops. Note the “>” symbol at the clock input.



Positive edge-triggered flip-flops

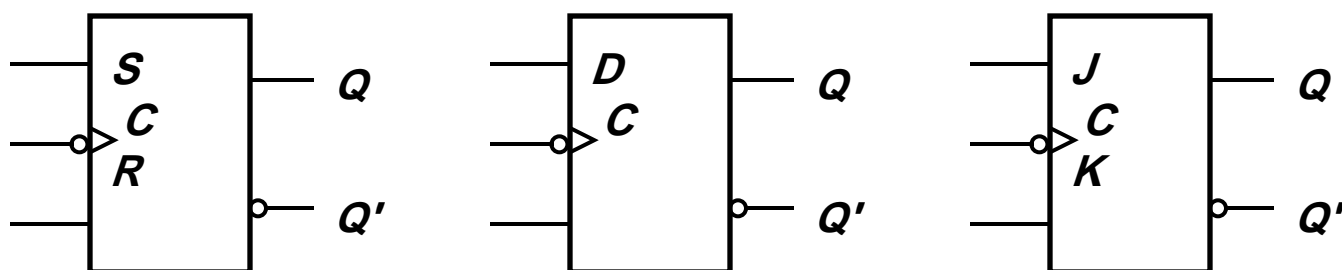

Negative edge-triggered flip-flops




S-R Flip-flop

- **S-R flip-flop**: on the triggering edge of the clock pulse,
 - ❖ $S=HIGH$ (and $R=LOW$) \Rightarrow SET state
 - ❖ $R=HIGH$ (and $S=LOW$) \Rightarrow RESET state
 - ❖ both inputs LOW \Rightarrow no change
 - ❖ both inputs HIGH \Rightarrow invalid
- Characteristic table of positive edge-triggered S-R flip-flop:

S	R	CLK	$Q(t+1)$	Comments
0	0	X	$Q(t)$	No change
0	1	\uparrow	0	Reset
1	0	\uparrow	1	Set
1	1	\uparrow	?	Invalid


X = irrelevant ("don't care")

\uparrow = clock transition LOW to HIGH

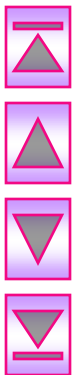




S-R Flip-flop

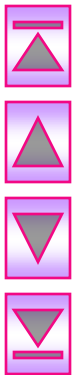- It comprises 3 parts:
 - ❖ a basic *NAND latch*
 - ❖ a *pulse-steering* circuit
 - ❖ a *pulse transition detector* (or *edge detector*) circuit
- The **pulse transition detector** detects a rising (or falling) edge and produces a very *short-duration spike*.





S-R Flip-flop


The pulse transition detector.

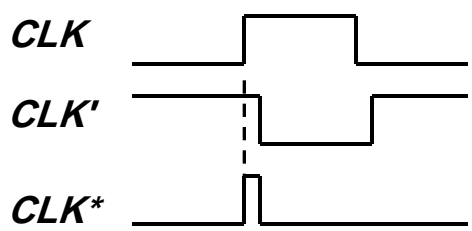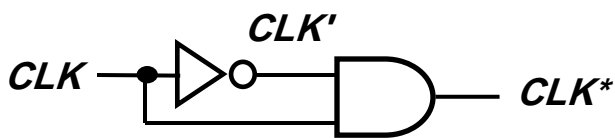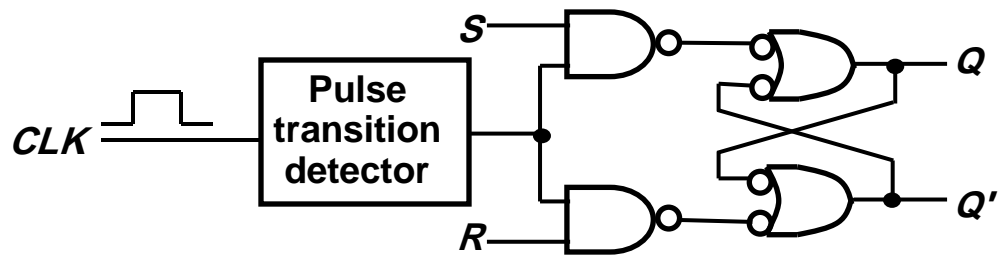

Positive-going transition
(rising edge)

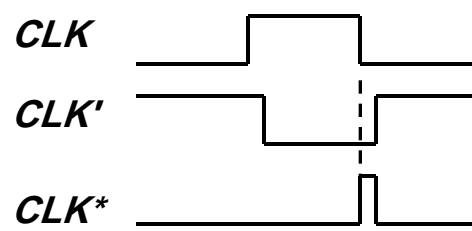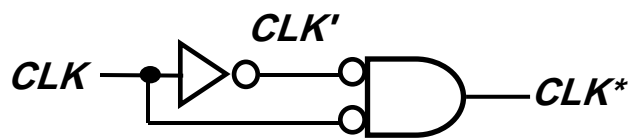


Negative-going transition
(falling edge)

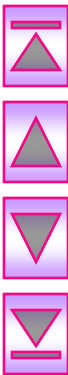

D Flip-flop

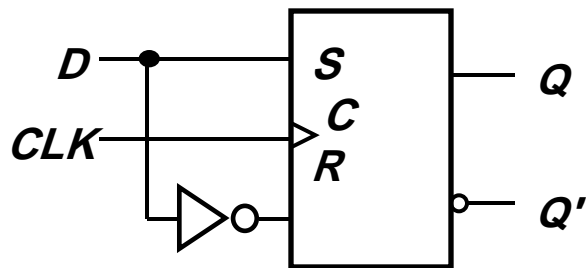- **D flip-flop**: single input D (data)
 - ❖ $D=\text{HIGH} \Rightarrow \text{SET state}$
 - ❖ $D=\text{LOW} \Rightarrow \text{RESET state}$
- Q follows D at the clock edge.
- Convert S-R flip-flop into a D flip-flop: add an inverter.




A positive edge-triggered D flip-flop formed with an S-R flip-flop.

D	CLK	$Q(t+1)$	Comments
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH


J-K Flip-flop

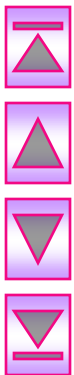- J-K flip-flop: Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a *toggle* state.
 - ❖ $J=HIGH$ (and $K=LOW$) \Rightarrow SET state
 - ❖ $K=HIGH$ (and $J=LOW$) \Rightarrow RESET state
 - ❖ both inputs LOW \Rightarrow no change
 - ❖ both inputs HIGH \Rightarrow toggle



J-K Flip-flop

- J-K flip-flop.

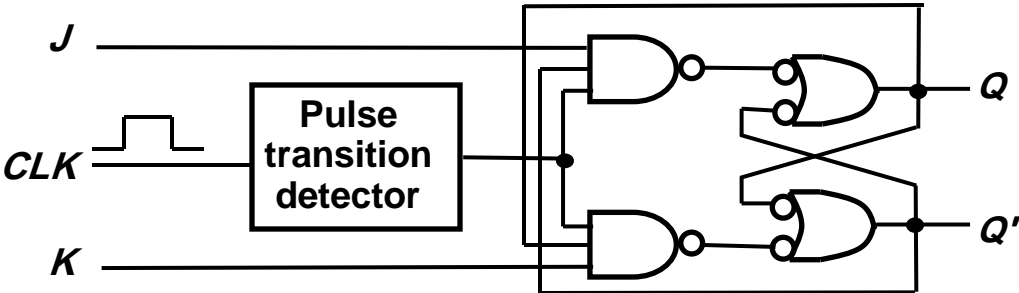


- Characteristic table.

J	K	CLK	Q(t+1)	Comments
0	0	↑	Q(t)	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	Q(t)'	Toggle


$$Q(t+1) = J.Q' + K'.Q$$

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

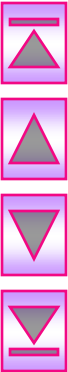

T Flip-flop

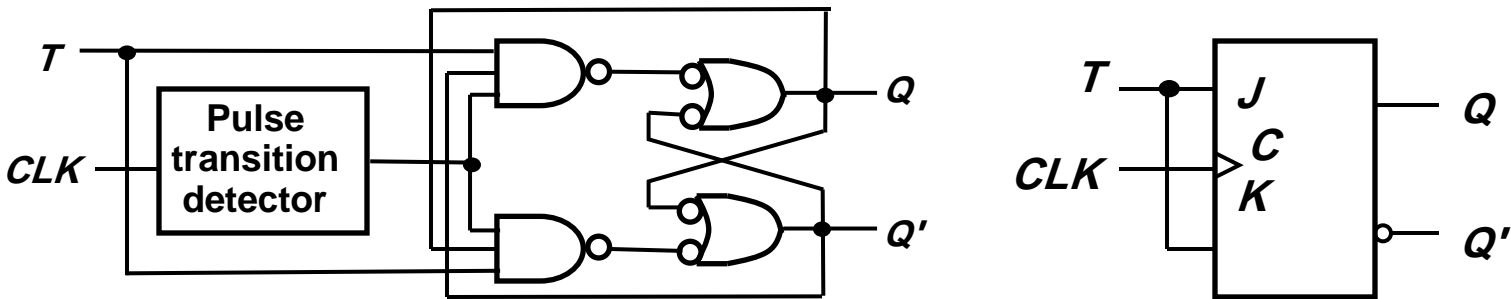- **T flip-flop**: single-input version of the J–K flip flop, formed by tying both inputs together.



- Characteristic table.

T	CLK	Q(t+1)	Comments
0	↑	Q(t)	No change
1	↑	Q(t)'	Toggle


Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = T.Q' + T'.Q$$

CLOCK PERIOD

**Clock period determines how fast the digital circuit operates.
How can we determine the clock period ?**

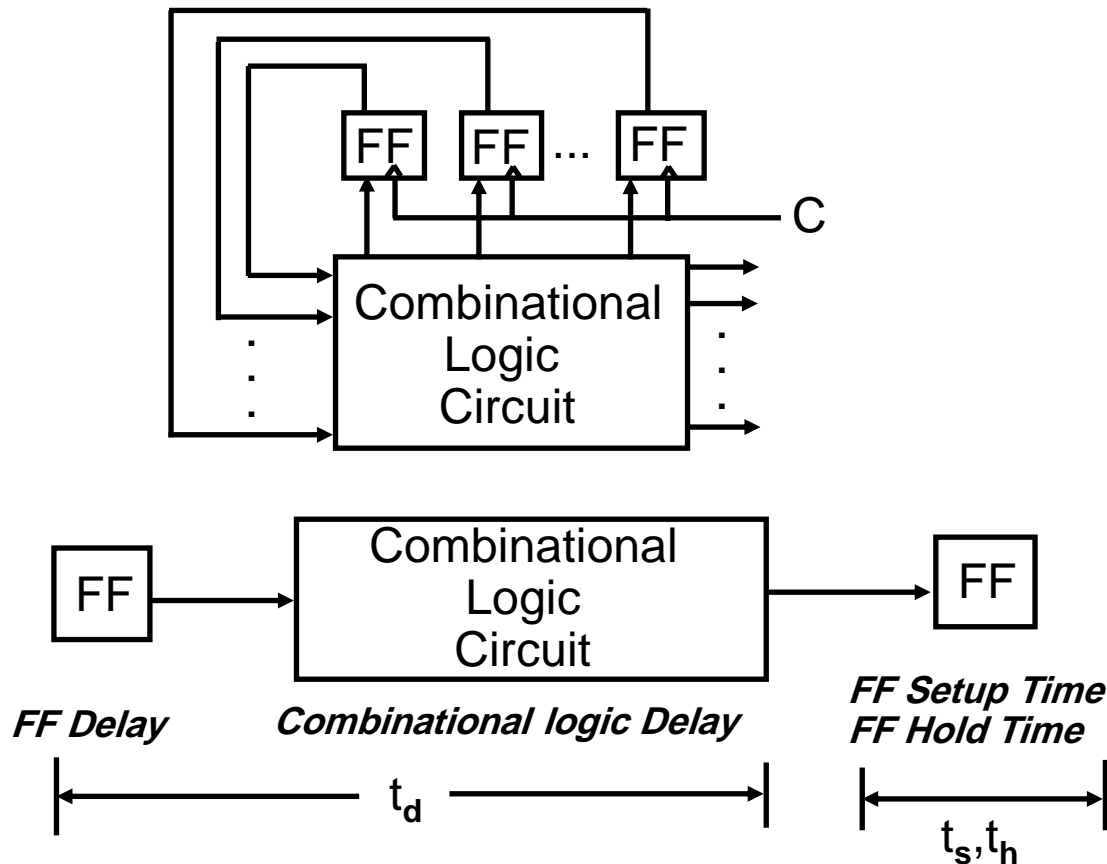
Usually, digital circuits are sequential circuits which has some flip flops




DESIGN EXAMPLE

Design Procedure:
Specification \Rightarrow State Diagram \Rightarrow State Table \Rightarrow
Excitation Table \Rightarrow Karnaugh Map \Rightarrow Circuit Diagram

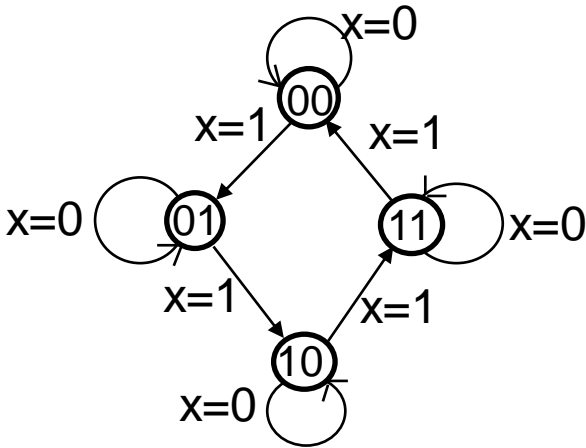
Example: 2-bit Counter \rightarrow 2 FF's




current state		input	next state		FF inputs			
A	B		A	B	Ja	Ka	Jb	Kb
0	0	0	0	0	0	d	0	d
0	0	1	0	1	0	d	1	d
0	1	0	0	1	0	d	d	0
0	1	1	1	0	1	d	d	1
1	0	0	1	0	d	0	0	d
1	0	1	1	1	d	0	1	d
1	1	0	1	1	d	0	d	0
1	1	1	0	0	d	1	d	1

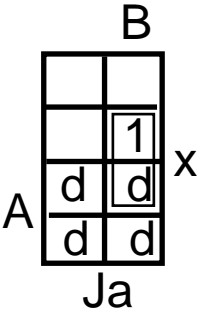


$Ja = Bx$

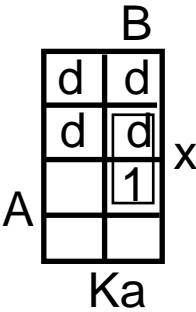


$Ka = Bx$

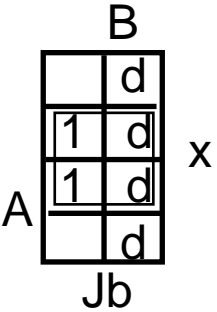


$Jb = x$

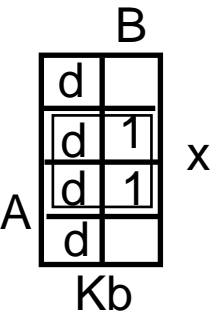


$Kb = x$

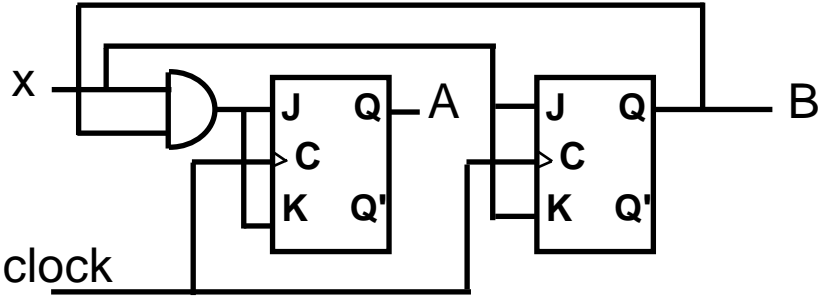


SEQUENTIAL CIRCUITS - Registers

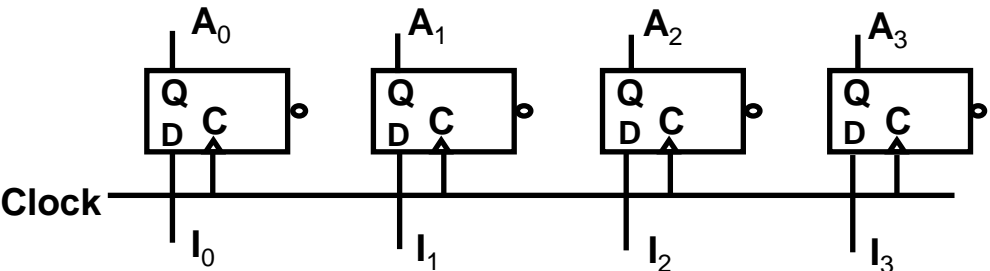


Shift Registers

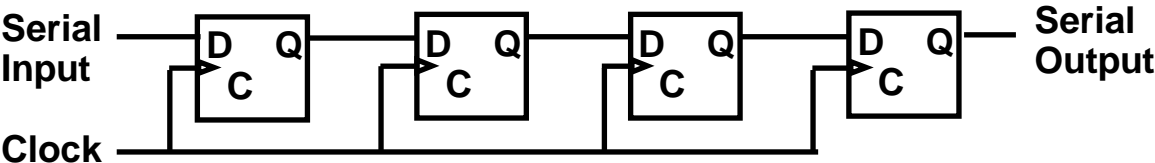

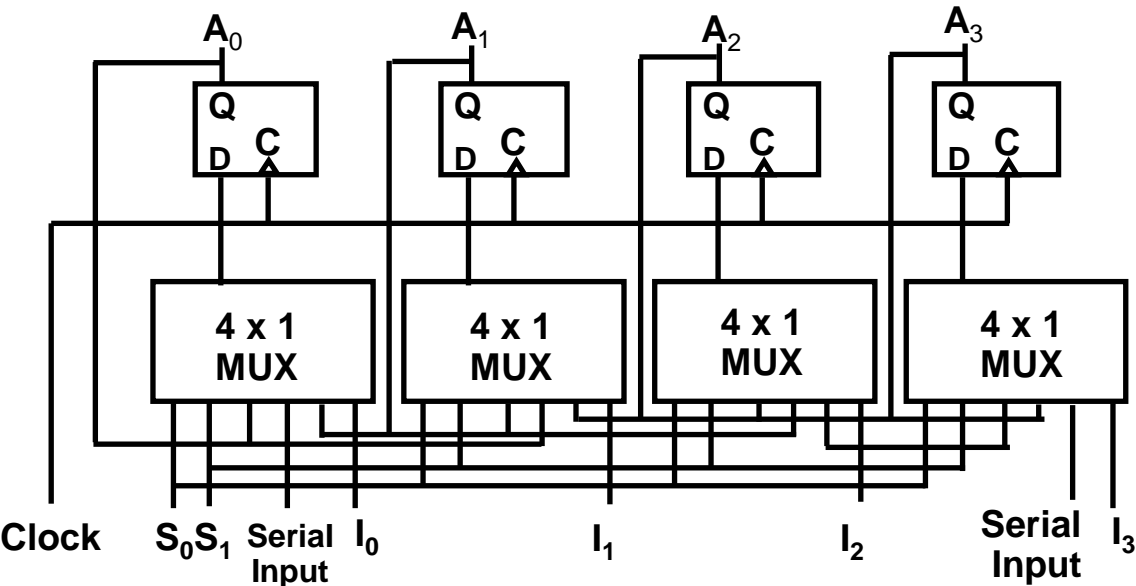Bidirectional Shift Register with Parallel Load




SEQUENTIAL CIRCUITS - Counters

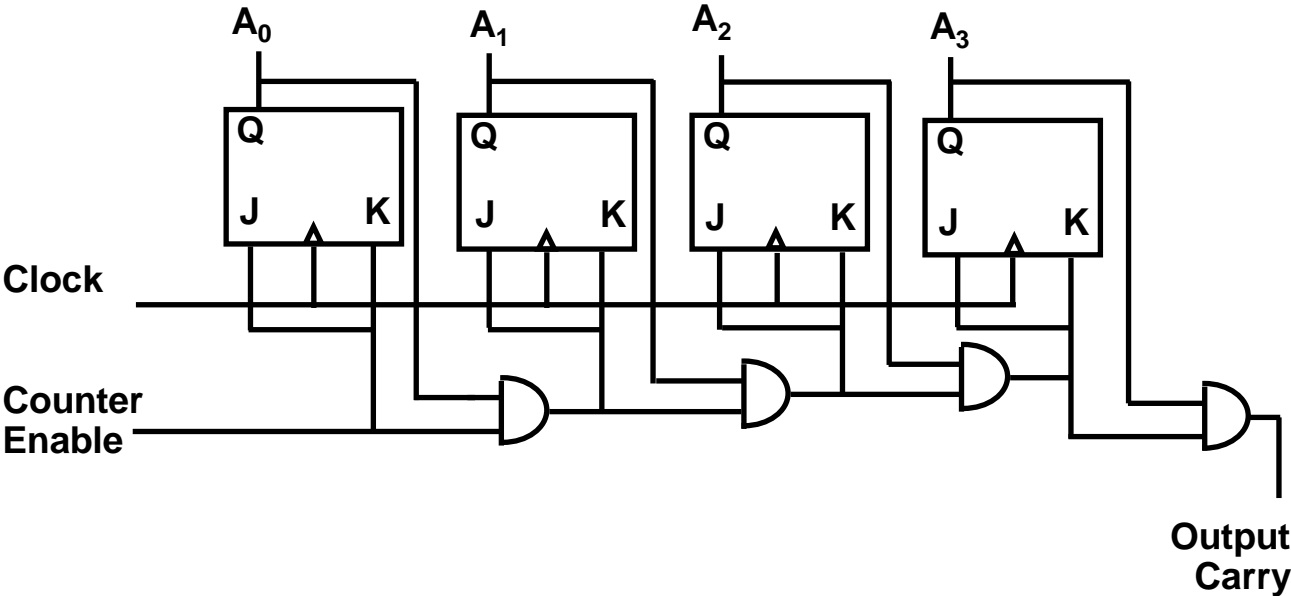

MEMORY COMPONENTS


Logical Organization

words
(byte, or n bytes)

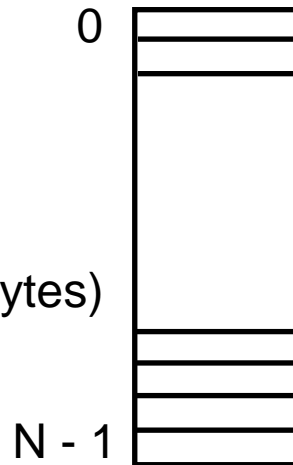

Random Access Memory

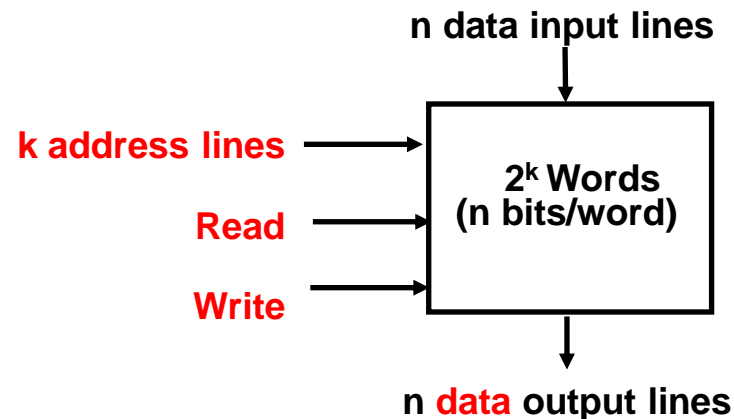- Each word has a unique address
- Access to a word requires the same time independent of the location of the word
- Organization




READ ONLY MEMORY(ROM)

Characteristics

- Perform read operation only, write operation is not possible
- Information stored in a ROM is made permanent during production, and cannot be changed
- Organization


k address input lines

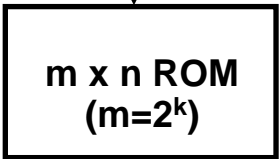

n data output lines

Information on the data output line depends only on the information on the address input lines.

--> Combinational Logic Circuit

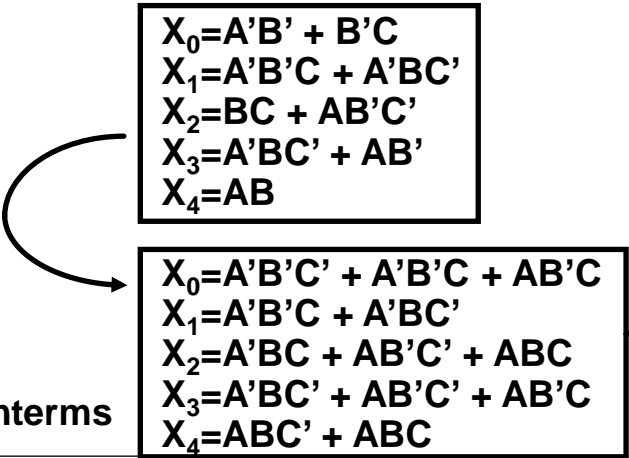

<i>address</i>	<i>Output</i>				
	ABC	X₀	X₁	X₂	X₃
000	1	0	0	0	0
001	1	1	0	0	0
010	0	1	0	1	0
011	0	0	1	0	0
100	0	0	1	1	0
101	1	0	0	1	0
110	0	0	0	0	1
111	0	0	1	0	1

TYPES OF ROM

ROM

- Store information (function) during production
- Mask is used in the production process
- Unalterable
- Low cost for large quantity production --> used in the final products

PROM (Programmable ROM)

- Store info electrically using PROM programmer at the user's site
- Unalterable
- Higher cost than ROM -> used in the system development phase
-> Can be used in small quantity system

EPROM (Erasable PROM)

- Store info electrically using PROM programmer at the user's site
- Stored info is erasable (alterable) using UV light (electrically in some devices) and rewriteable
- Higher cost than PROM but reusable --> used in the system development phase. Not used in the system production due to erasability

INTEGRATED CIRCUITS

Classification by the Circuit Density

- SSI -** several (less than 10) independent gates
- MSI -** 10 to 200 gates; Perform elementary digital functions;
Decoder, adder, register, parity checker, etc
- LSI -** 200 to few thousand gates; Digital subsystem
Processor, memory, etc
- VLSI -** Thousands of gates; Digital system
Microprocessor, memory module

Classification by Technology

- TTL -** Transistor-Transistor Logic
Bipolar transistors
NAND
- ECL -** Emitter-coupled Logic
Bipolar transistor
NOR
- MOS -** Metal-Oxide Semiconductor
Unipolar transistor
High density
- CMOS -** Complementary MOS
Low power consumption